

Lecture 20: Memory Technology

COS 471a, COS 471b / ELE 375

Computer Architecture and Organization

Princeton University
Fall 2004

Prof. David August

1

Program Notes

Homework #3

- Due December 6th (Monday)
- Out this week

Reading

- Chapters 1-8, A-C

Today

- Short Lecture


2



Old Stuff Revisited

Mercury Delay Line Memory




 
Maurice Wilkes, in 1947, with
first mercury tank memories
built for EDSAC.



4


Core Memory

16K!

    

- Theory of operation
- Threaded by hand!
- The Lifesaver connection
- Refresh



Static RAM (SRAM)

 

- SRAM - Fast, but not the most dense (better than core!)
- Chip select can be viewed as another address line
- Din and Dout are often combined to save pins
 - Need output enable (OE_L - enable low)
 - Need write enable (WE_L - enable low)
- Don't assert both write enable and output enable
 - Result is unknown.
 - This is bad.
 - Don't do it!!!

The Transistor Makes It Possible! Static RAM (SRAM) Cell


6-Transistor SRAM Cell

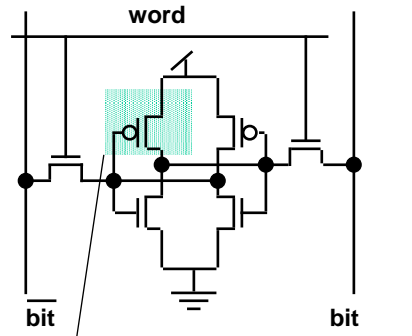 

- Write:
1. Drive bit lines (bit=1, bitbar=0)
 2. Select row
- Read:
1. Precharge bit and bitbar to Vdd
 2. Select row
 3. Cell pulls one line low
 4. Sense amp on column detects difference between bit and bitbar


Why is it Static?

Typical SRAM Organization

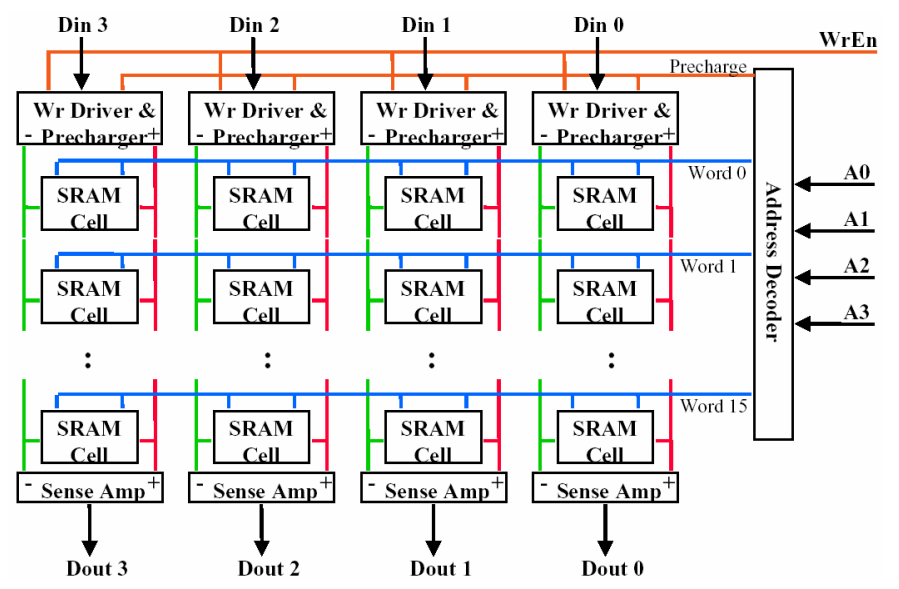


Three-State Buffers

Avoid HUGE MUX using three-state buffers

 


9

Typical SRAM Timing

 

Write Timing:


Read Timing:

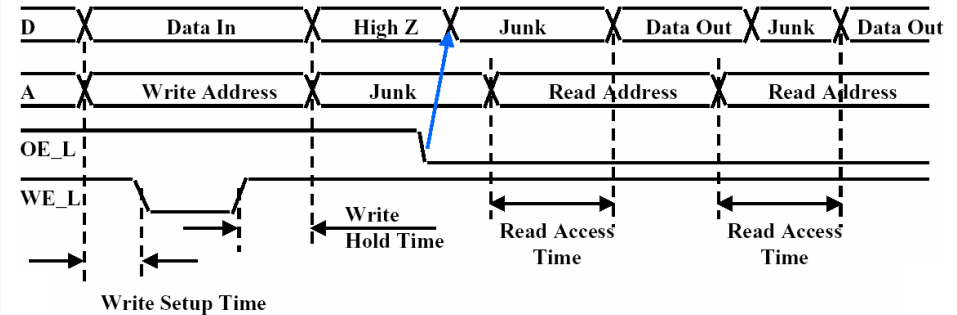

10


Dynamic RAM (DRAM)

 - Slower, cheaper, more dense than SRAM
- Dynamic?



11

Dynamic RAM Cell DRAM

 

Write:

1. Drive bit line
2. Select row/word line

Read:


1. Precharge bit line to Vdd
2. Select row/word line
3. Cell and bit line share charge
4. Sense (sense amp can detect changes of ~10-100k electrons)
5. Write: restore the value

Refresh (capacitor leaks):

1. Just do a dummy read to every cell.


12

Classical DRAM Organization (Square)

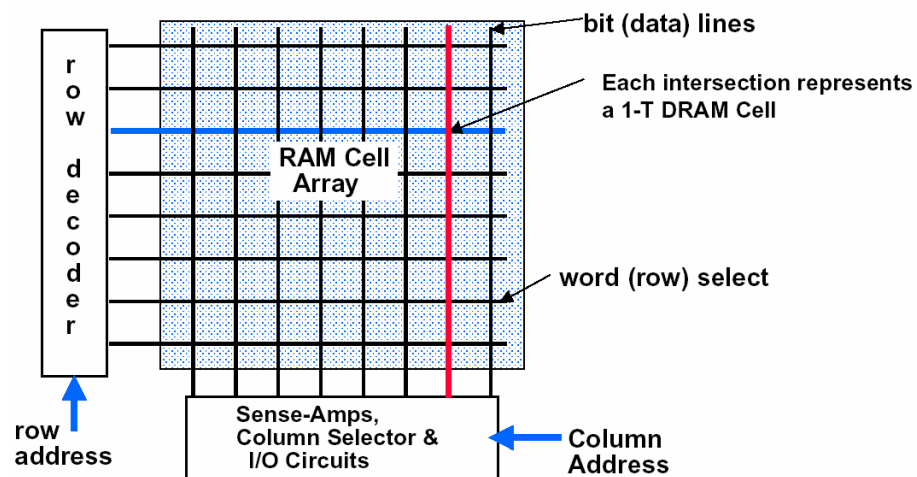


13

4Mx1 DRAM Organization

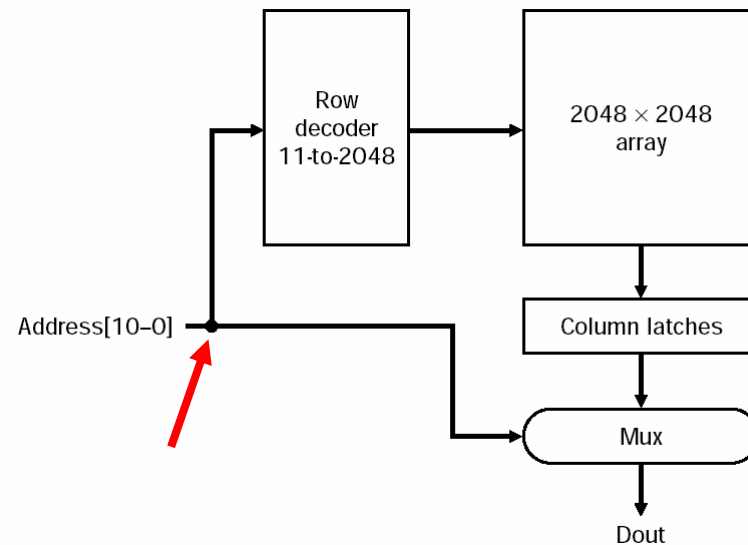

14


Logic Diagram of a Typical DRAM

 

- Row and column addresses share the same pins (A)
 - RAS_L goes low: Pins A are latched in as row address
 - CAS_L goes low: Pins A are latched in as column address
 - RAS/CAS edge-sensitive
- Din and Dout share the same pins (D)
- Control Signals (RAS_L, CAS_L, WE_L, OE_L) typically active low


15

DRAM Read Timing

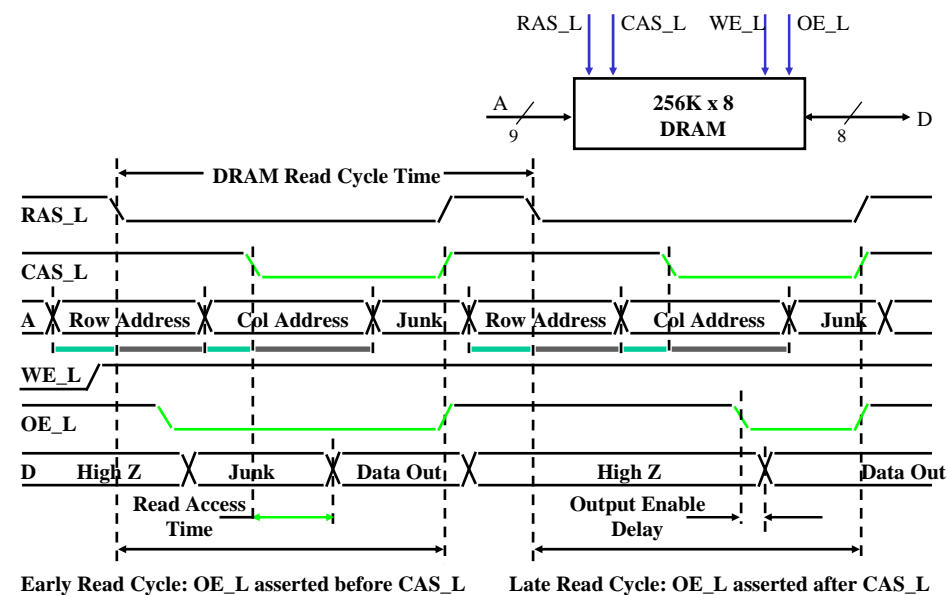

16


DRAM Write Timing

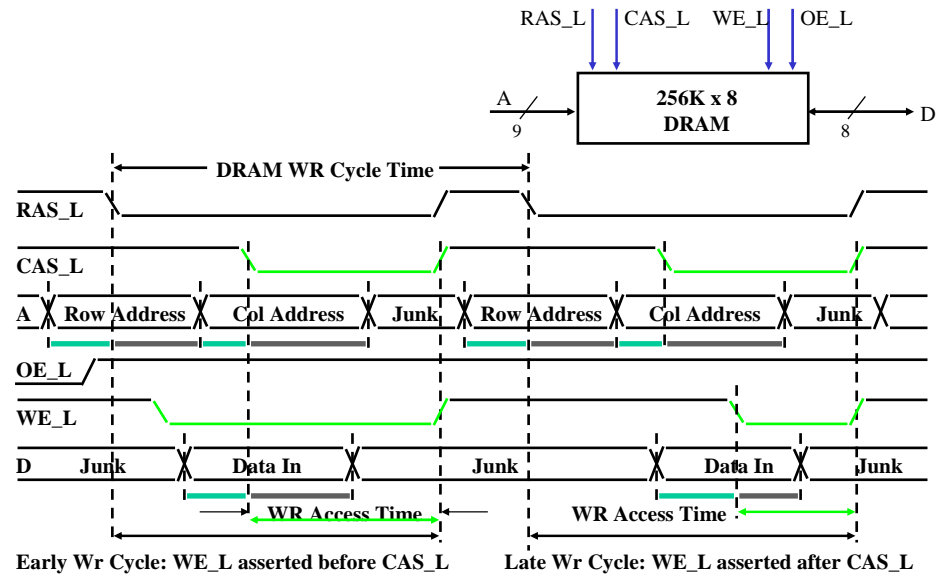


17

Increasing Bandwidth - Interleaving

Access Pattern without Interleaving:

 


Access Pattern with 4-way Interleaving:

 

18

"New" DRAMs

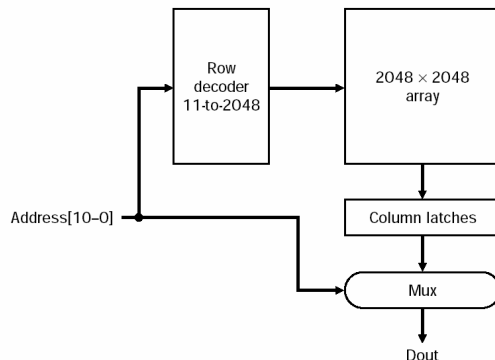- For decades, DRAM Interface was stable (RAS, CAS, etc.)
- Only in past decade has it begun to evolve again
 - Especially in systems with few DRAM chips
 - Bandwidth/Throughput
 - Ease of design
- Two key contenders:
 - Synchronous DRAM
 - Rambus DRAM



19

Summary

- DRAM à slow, cheap, dense
- Good for BIG main memory
 - Must be refreshed
- SRAM à fast, expensive, not very dense
- Good choice for fast memory like caches!
 - Holds state while power applied
- Memory hierarchy to get the best of both!

Enjoy Your Thanksgiving Break!

20